


#### Capacitors, Buzzer and Comparator


Instructed By: Mr. Supun Dissanayaka

Bhavat Ngamdeevilaisak

# Capacitor


#### Capacitor: How it is made...

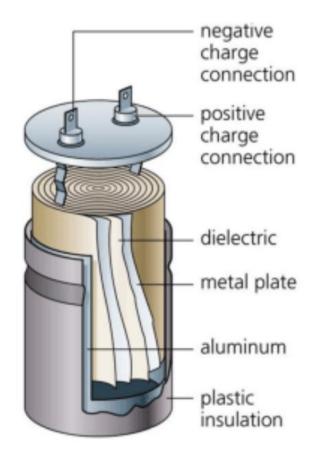

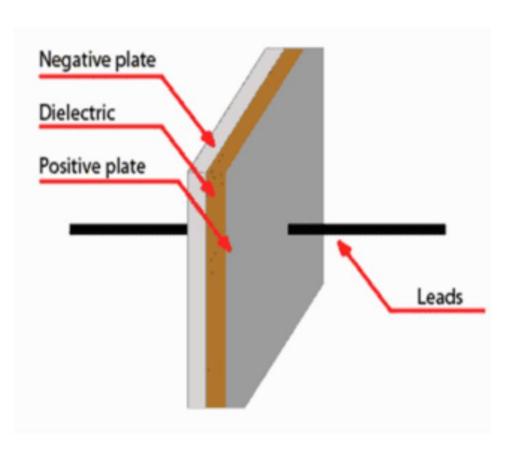


The structure of a real capacitor


# Capacitor: Current & Voltage behavior

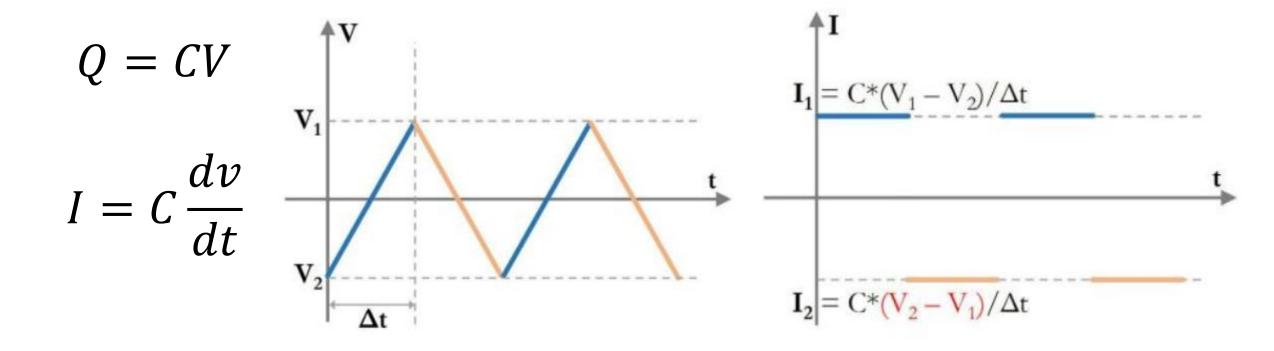

# Capacitor: Current & Voltage behavior

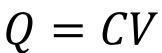

$$I = C \frac{dv}{dt}$$

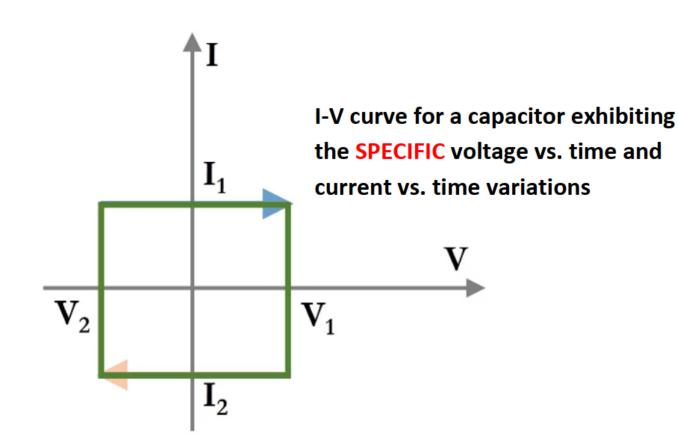


### Capacitor: Series and Parallel

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$


Series circuit  $C_1$   $C_2$ 

$$C_{eq} = C_1 + C_2$$


Parallel circuit

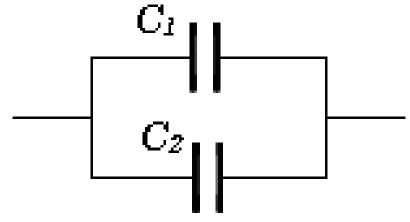

## Capacitor: Series and Parallel

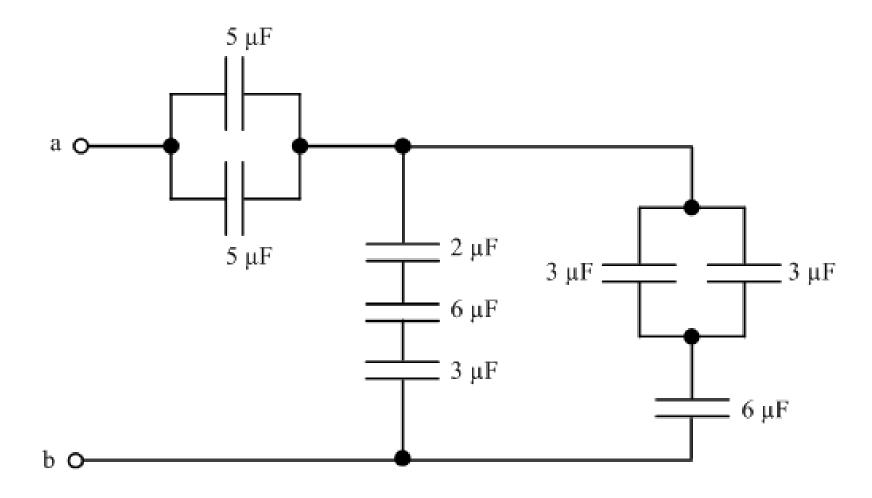


#### Buzzers

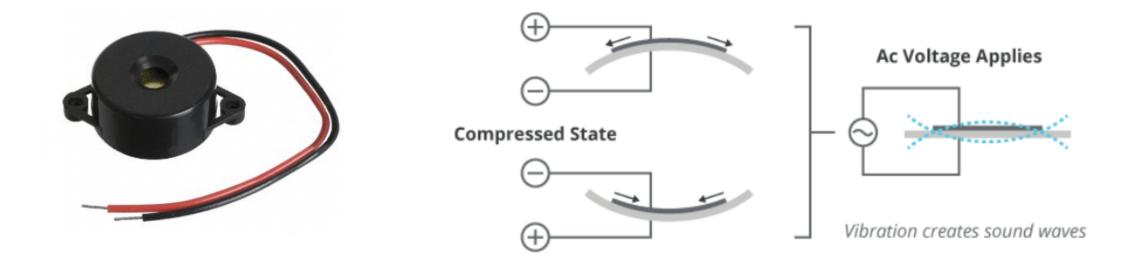

Piezo buzzer

# Buzzers (Contd.)



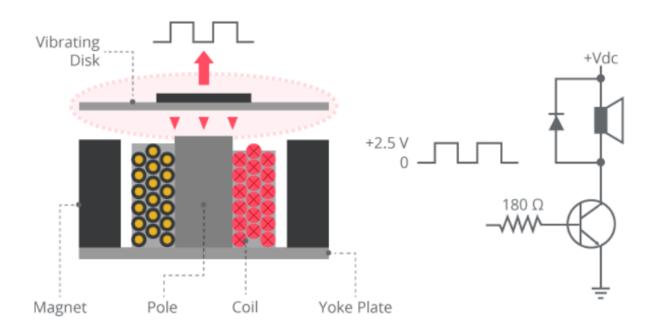

Magnetic buzzer

#### Push buttons




Push button

#### Rules of Op-Amp

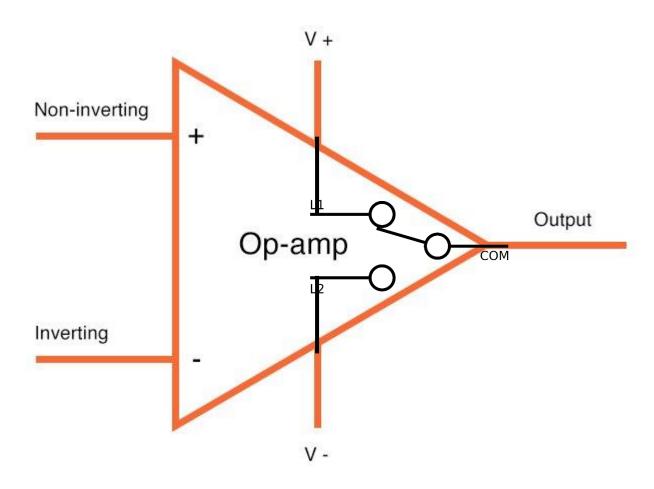
- 1. The Op-Amp will try to keep the same voltage on both inputs
- 2. No current can be flow in or out of the inputs of the Op-Amp.


Vout = (Non inverting - inverting) \* gain Non-inverting + Using Op-Amp as a comparator Output Op-amp Inverting

You can think of it likes a switch that switch the output to V+ or V-depending on the input condition




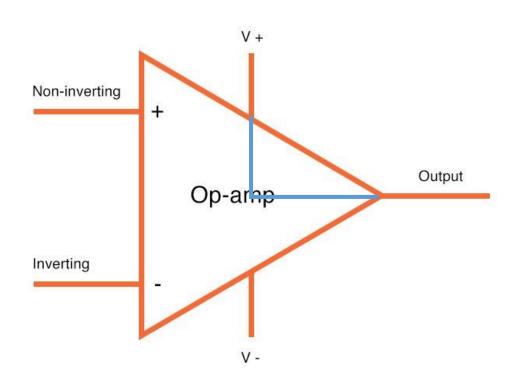
If V at non-inverting input is **greater** than inverting input output will be connected to **V+** 



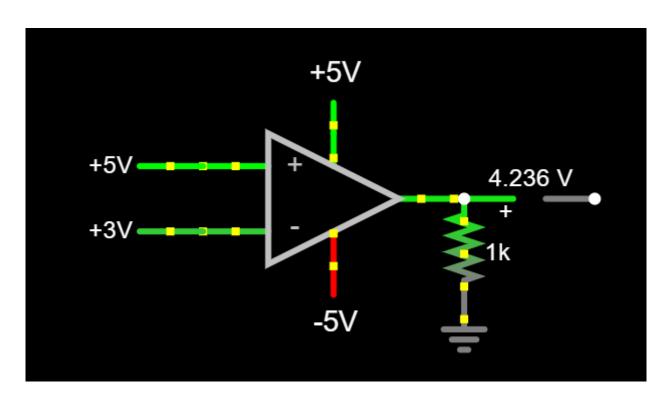

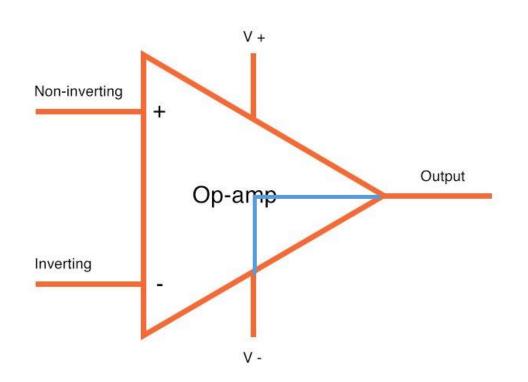If V at non-inverting input is <u>less</u> than inverting input output will be connected to **V**-



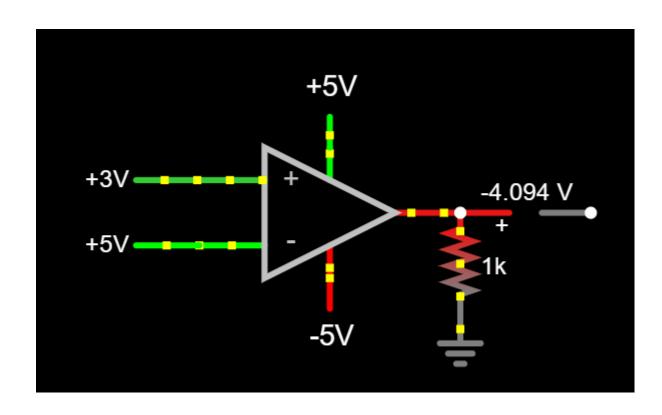

# Thanks for listening...