





I-V Characteristics, Kirchhoff's laws and Resistor Applications


Instructed By: Supun Dissanayaka
Bhavat Ngamdeevilaisak

Ohm's law

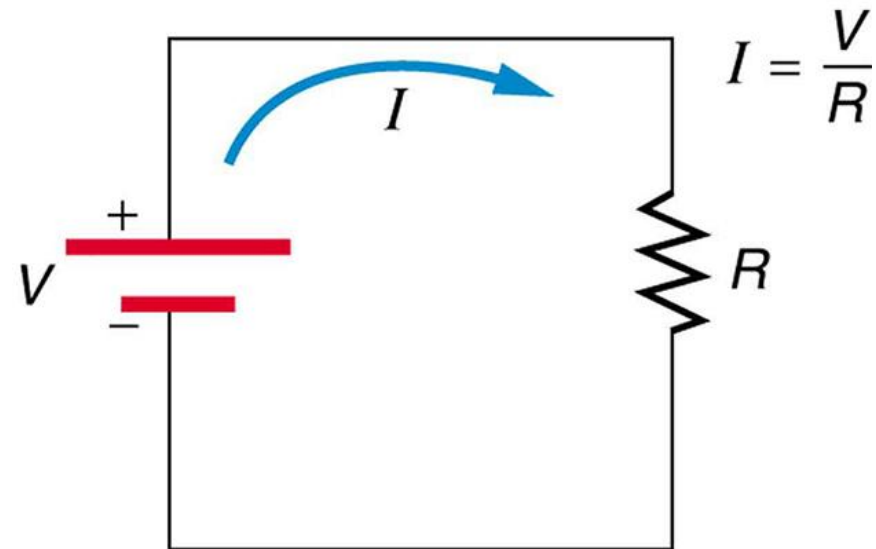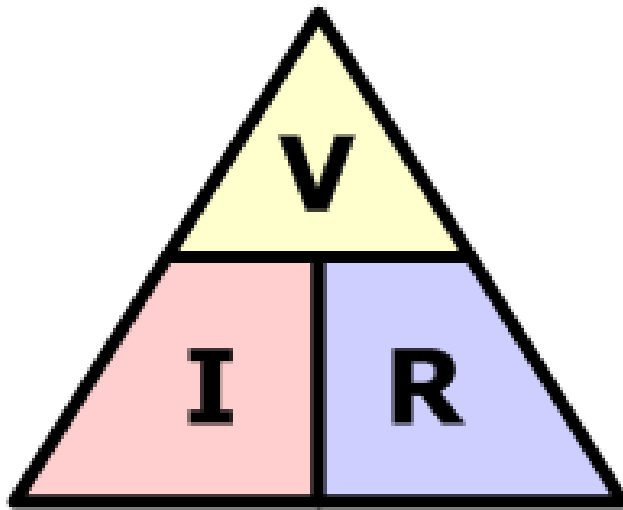
In an electrical circuit, the current passing through most materials is directly proportional to the potential difference applied across them.



I-V curves of a resistor

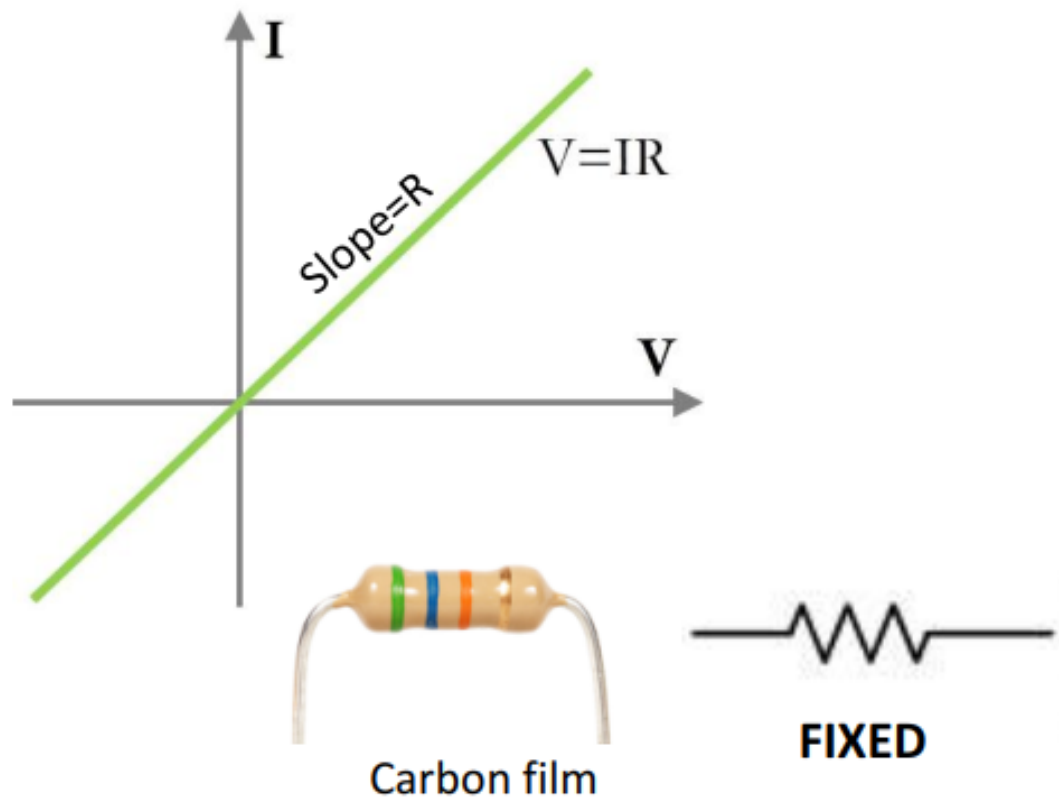


Ideal resistor

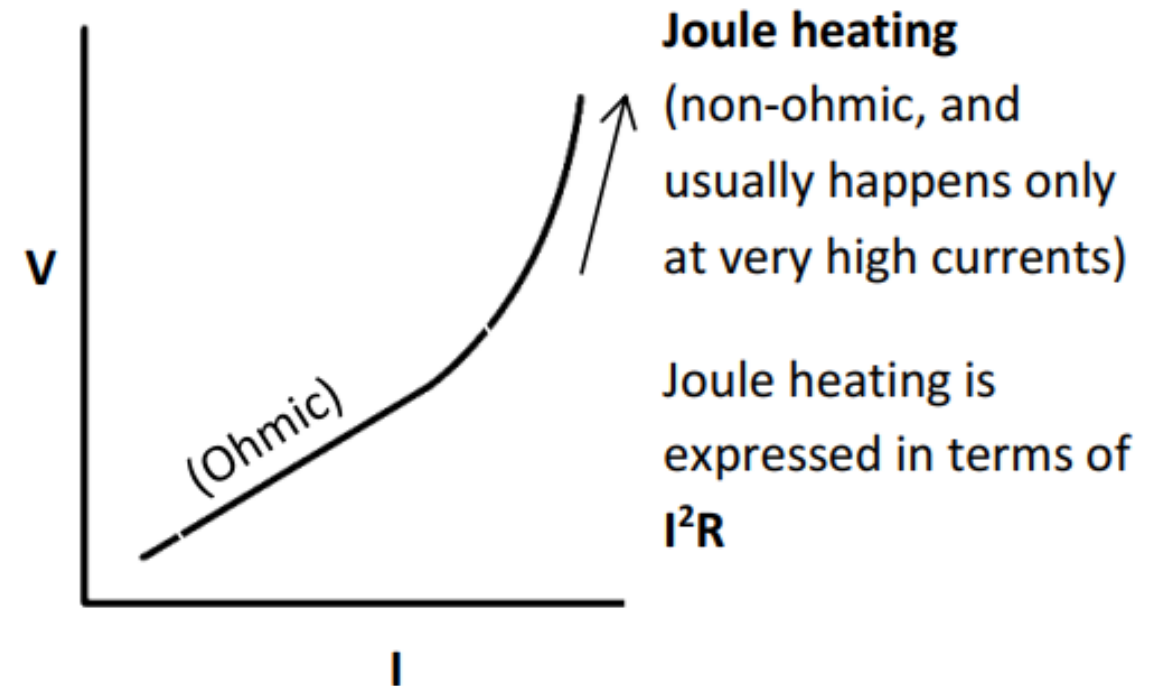

Note: Here V and I axis are switched

Non-ideal resistor

Usage of Ohmic heating

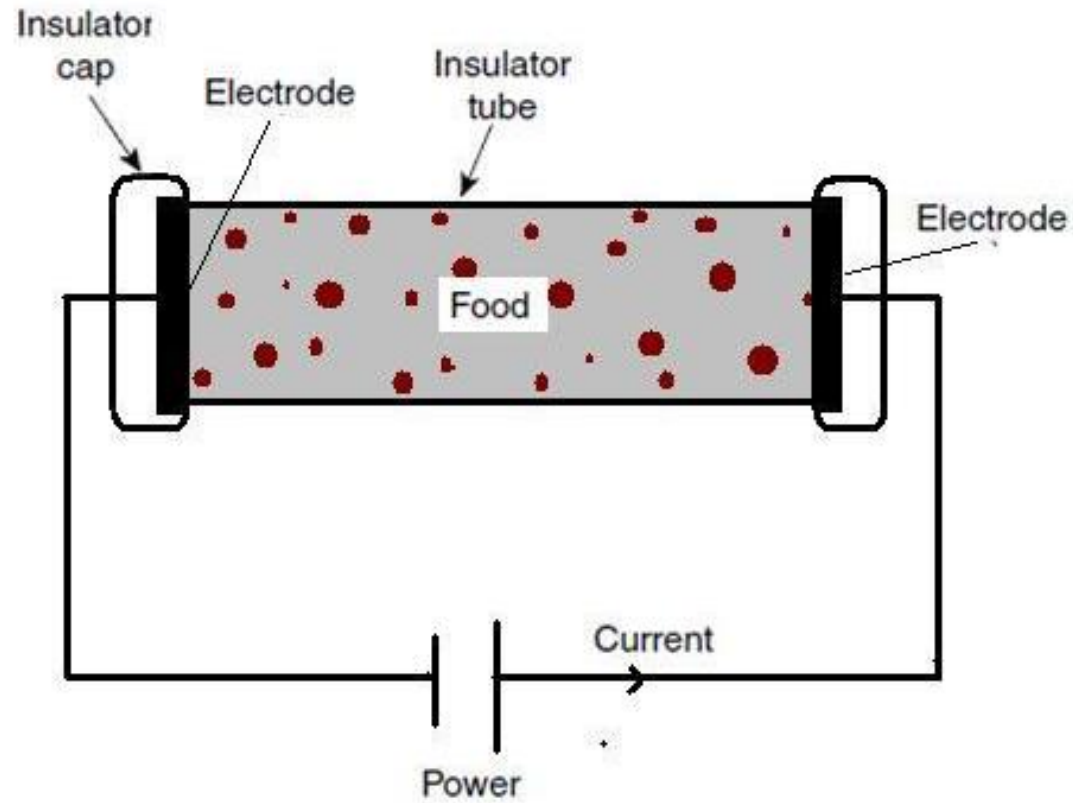

Food preservation




Ohmic heater

I-V curves of a variable resistor





Variable resistor

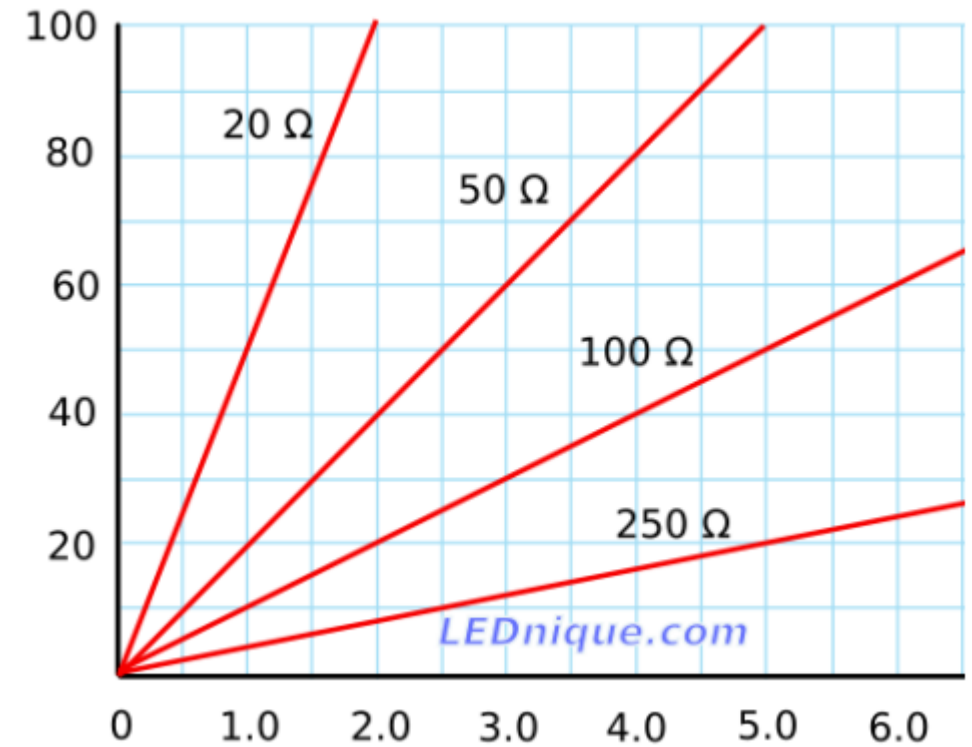

Variable resistor I-V curve


Variable resistor: Rheostat

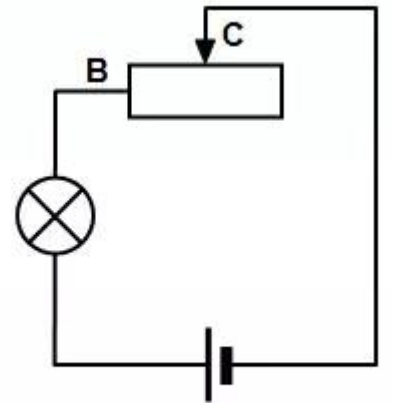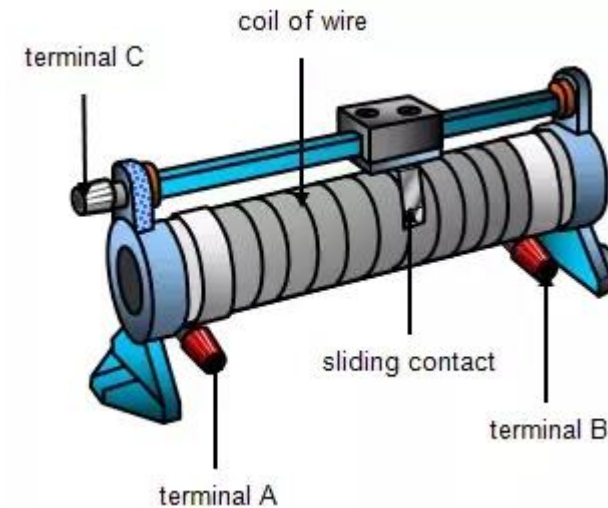


Rheostat function on a circuit

Resistor configuration




Series

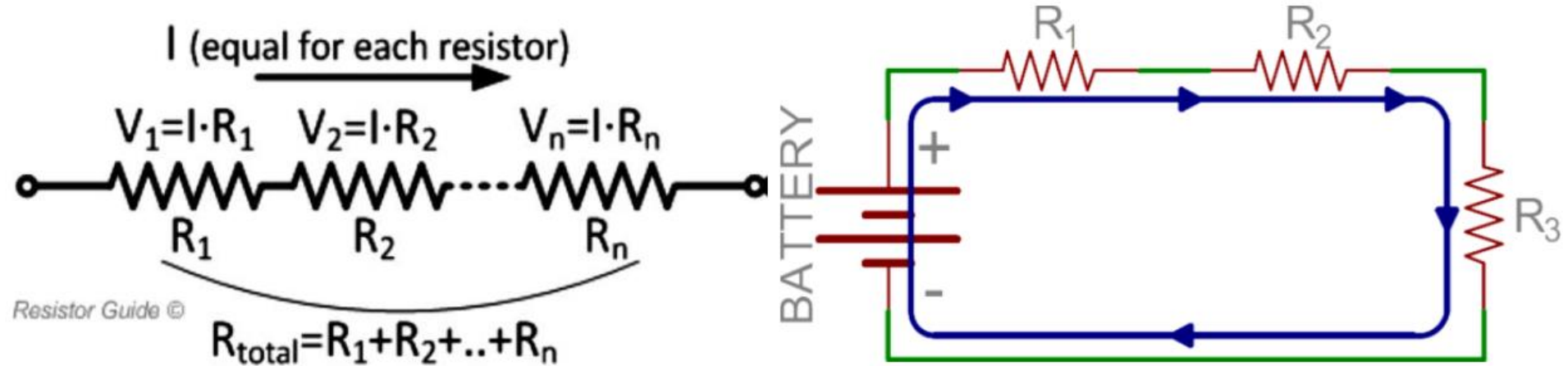


Parallel

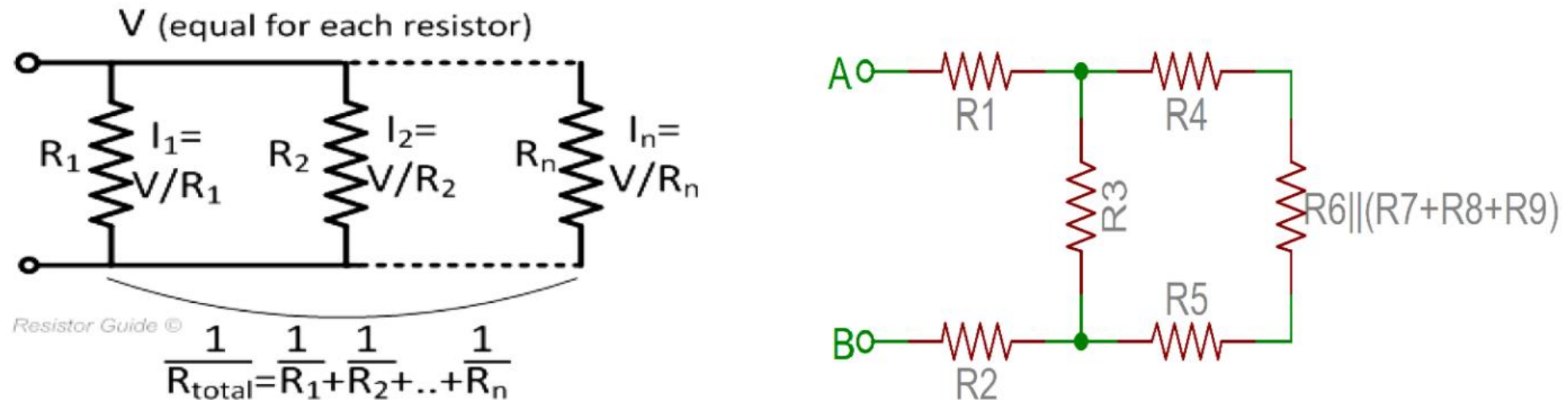

Light Dependent Resistors (LDR)

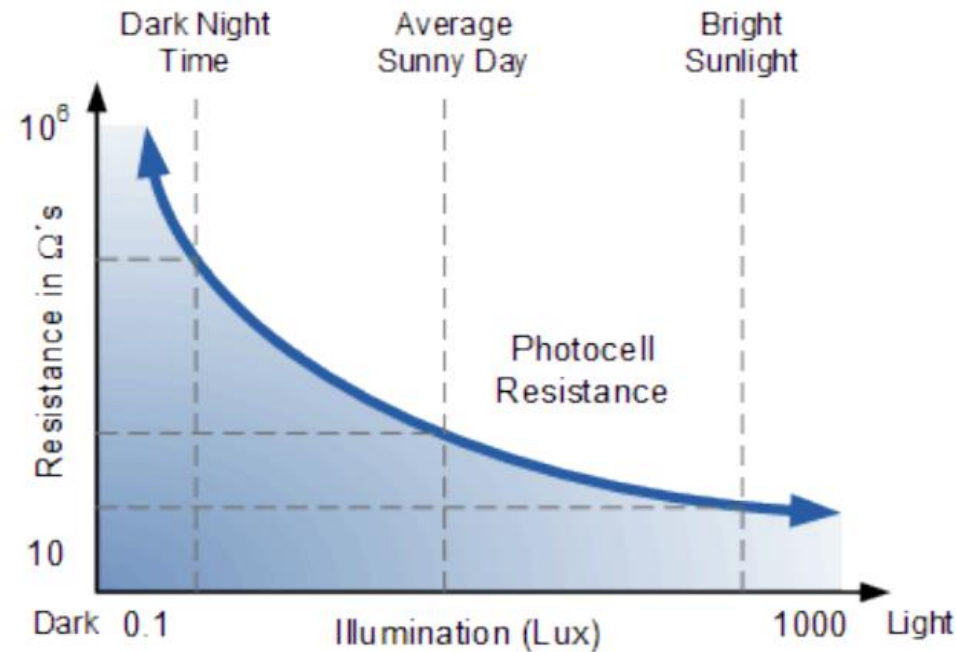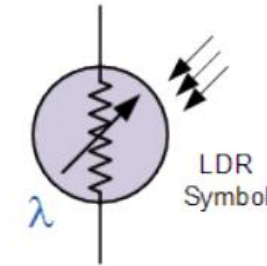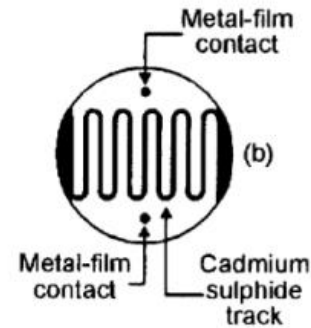

Voltage divider

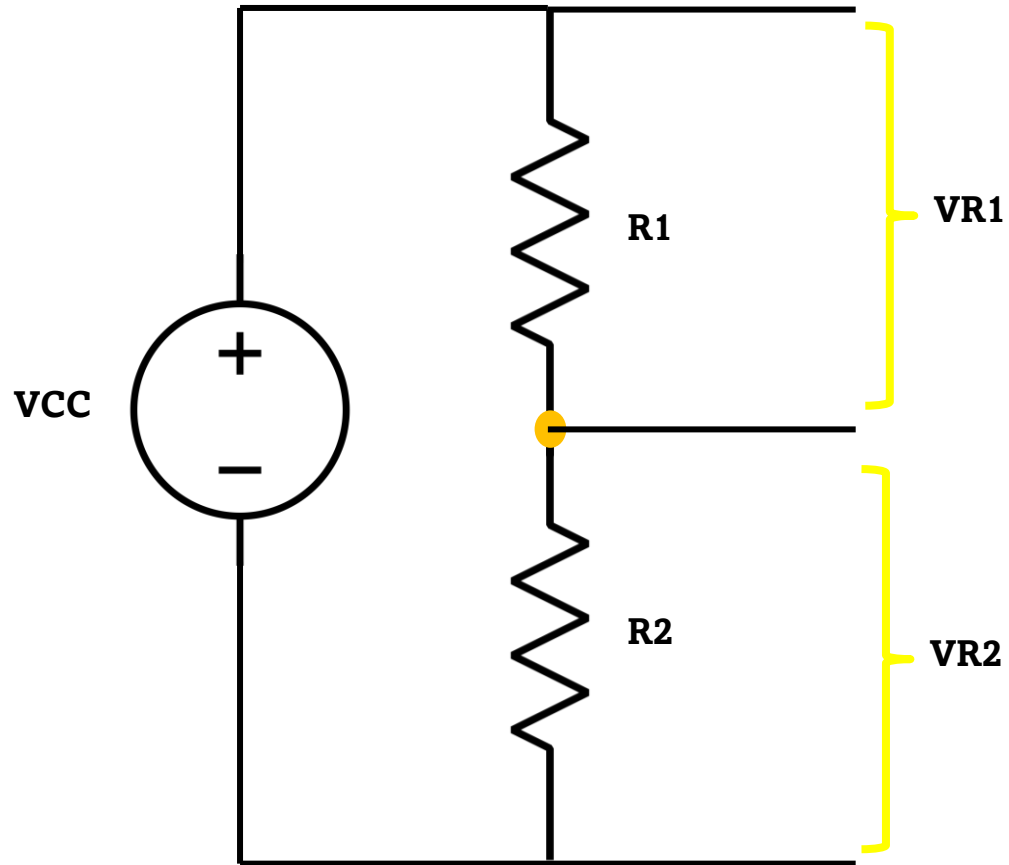


The voltage is depended on it's own resistance

$$V_{R1} = V_{CC} \times \left(\frac{R_1}{R_1 + R_2} \right)$$

$$V_{R2} = V_{CC} \times \left(\frac{R_2}{R_1 + R_2} \right)$$


Kirchoff's Law

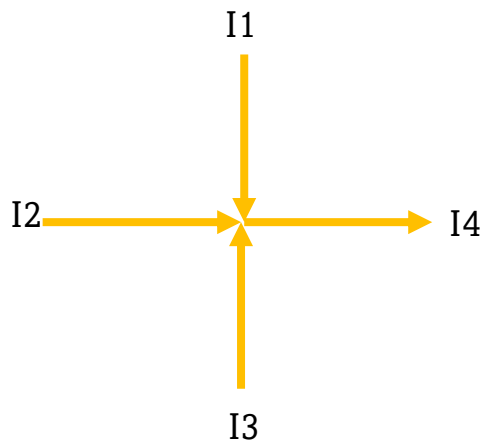

$$\text{KCL} : I_{in} = I_{out}$$

$$\text{KCL} : I_1 + I_2 + I_3 = I_4$$

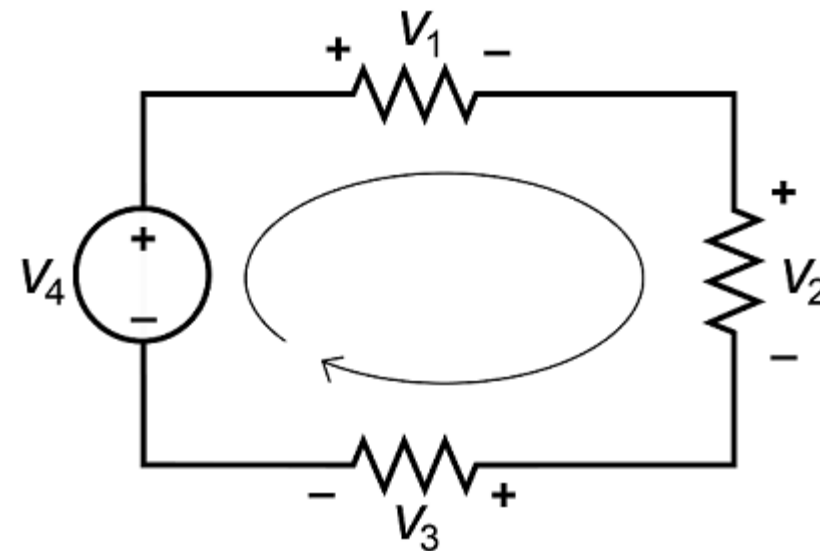The sum of the current entering any point is equal to the sum of the current leaving the same point





$$\text{KVL} : \sum V = 0$$

$$\text{KVL} : V_1 + V_2 + V_3 = V_4$$

The sum of the voltage in any close loop is equal to zero


Nodal analysis

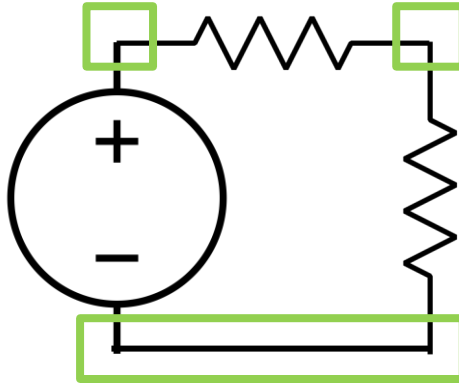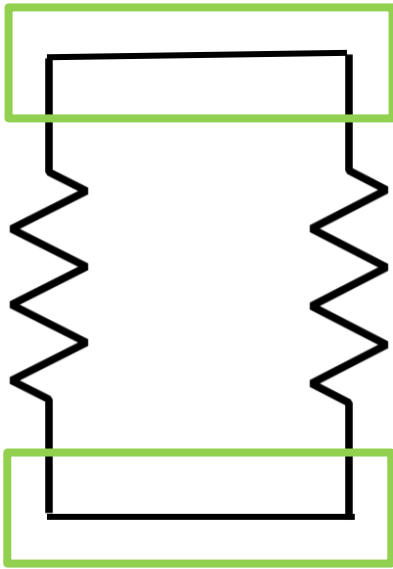The connection point between two or more components




Nodal analysis

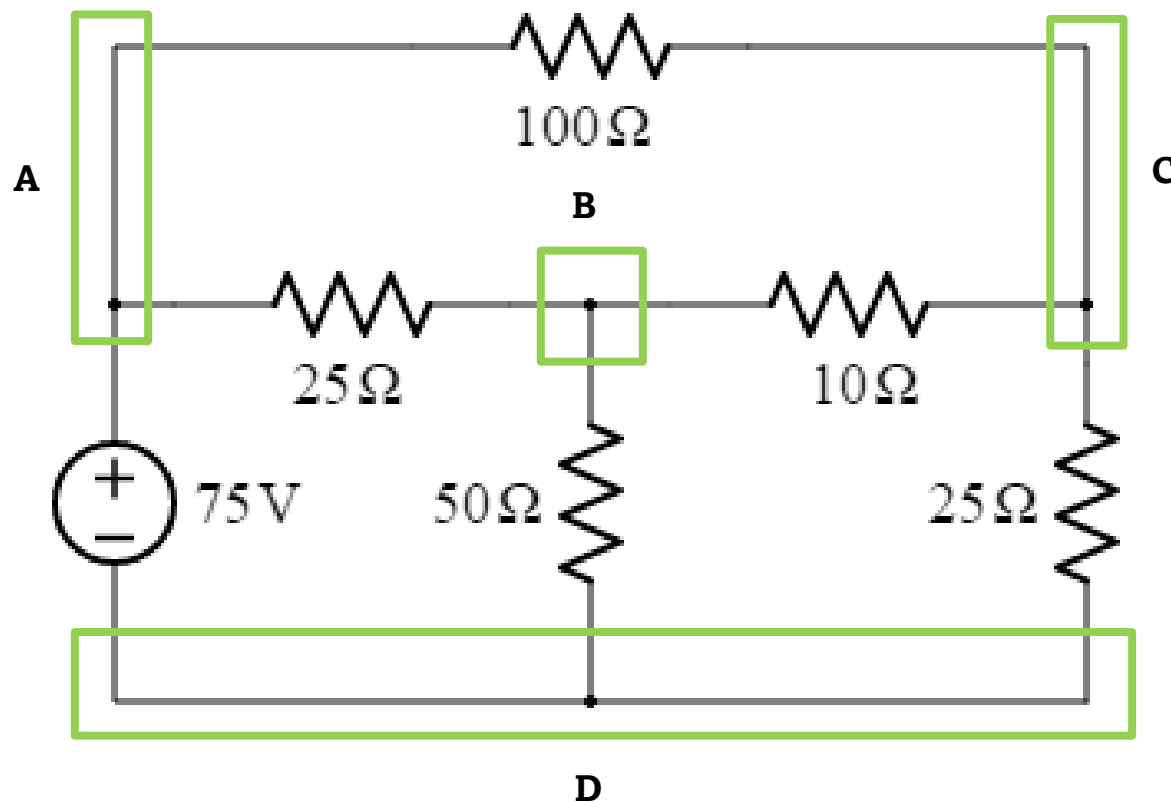The connection point between two or more components




Nodal analysis

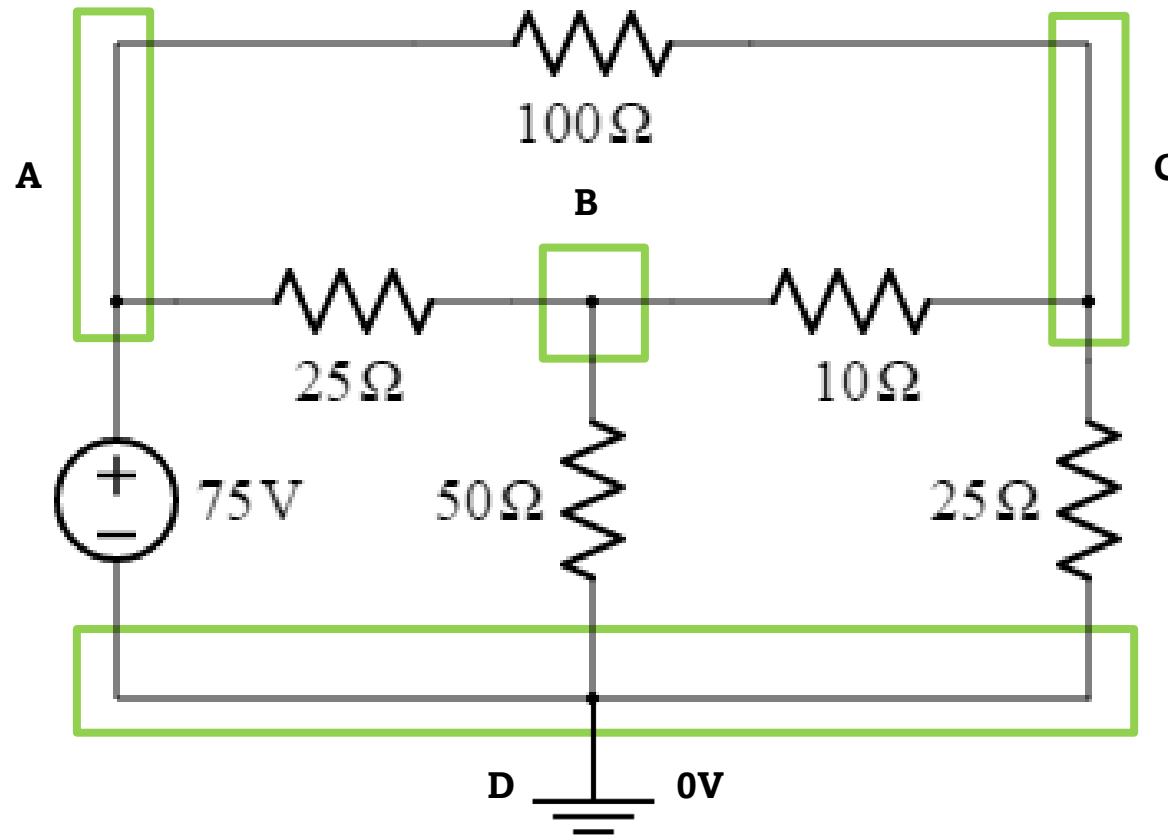STEP 1: Select 1 node as ground (Reference point)




Nodal analysis

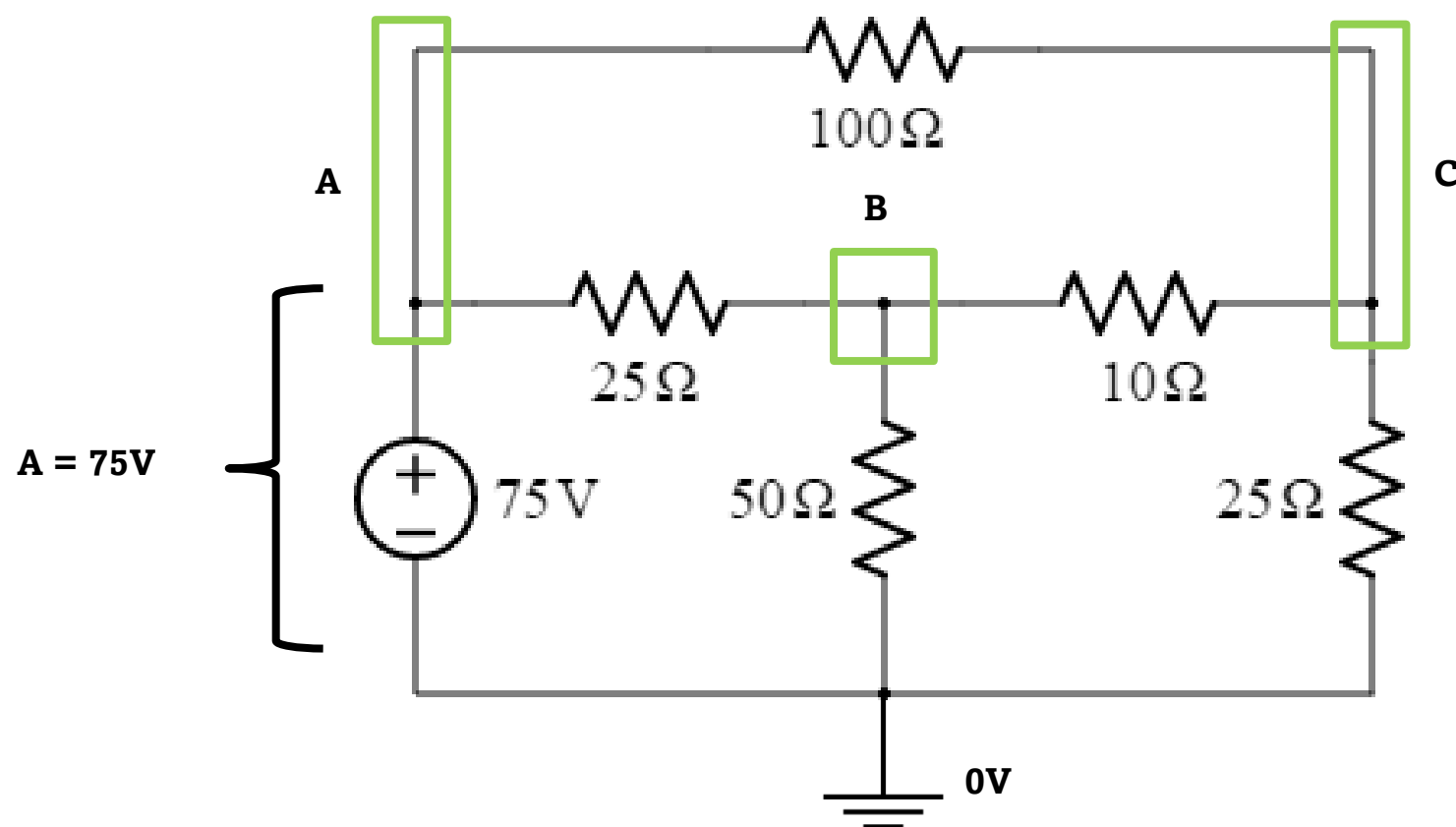STEP 2: Extract the most information possible from the circuit to minimize the numbers of analysis.



Nodal analysis

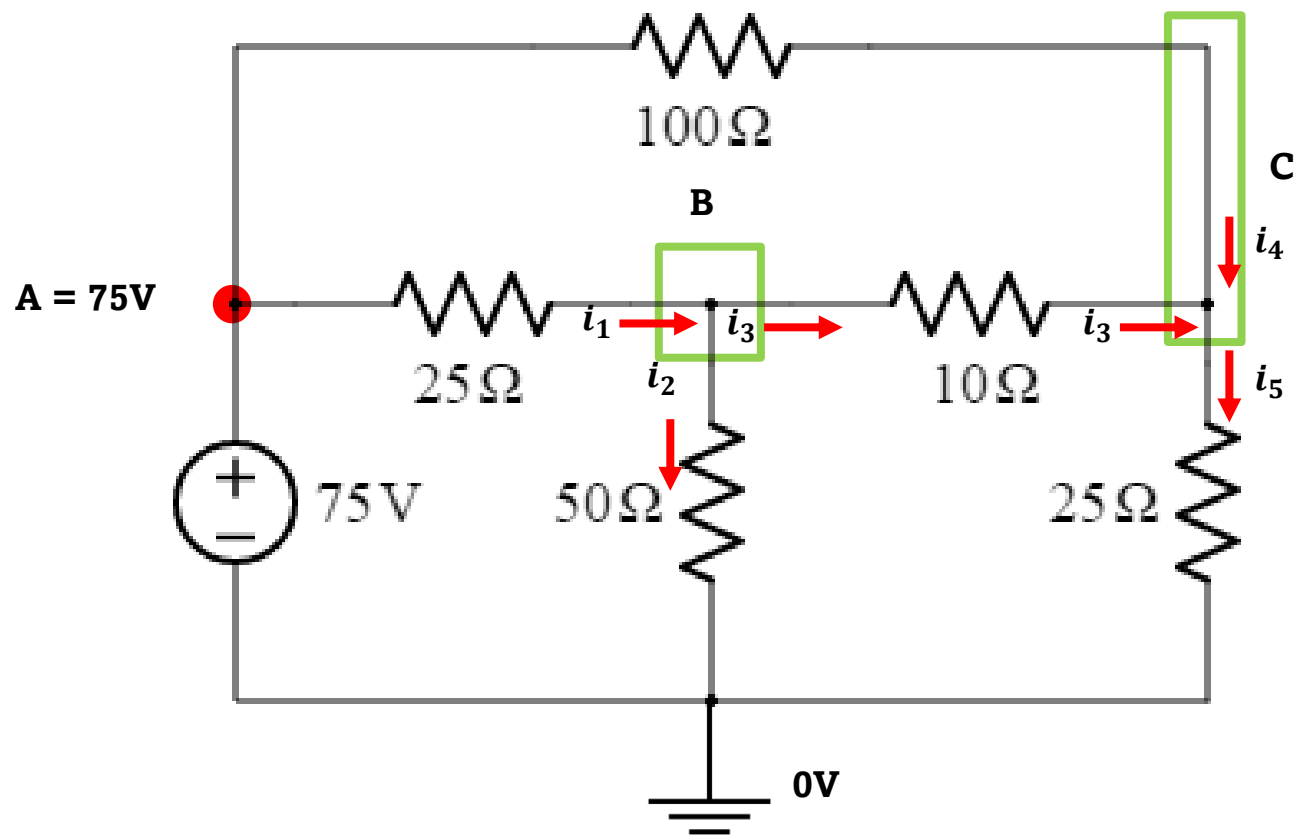STEP 3: Apply the KCL at the remaining nodes




$$\text{@node B: } i_1 = i_2 + i_3$$

$$\text{@node C: } i_5 = i_3 + i_4$$

Nodal analysis

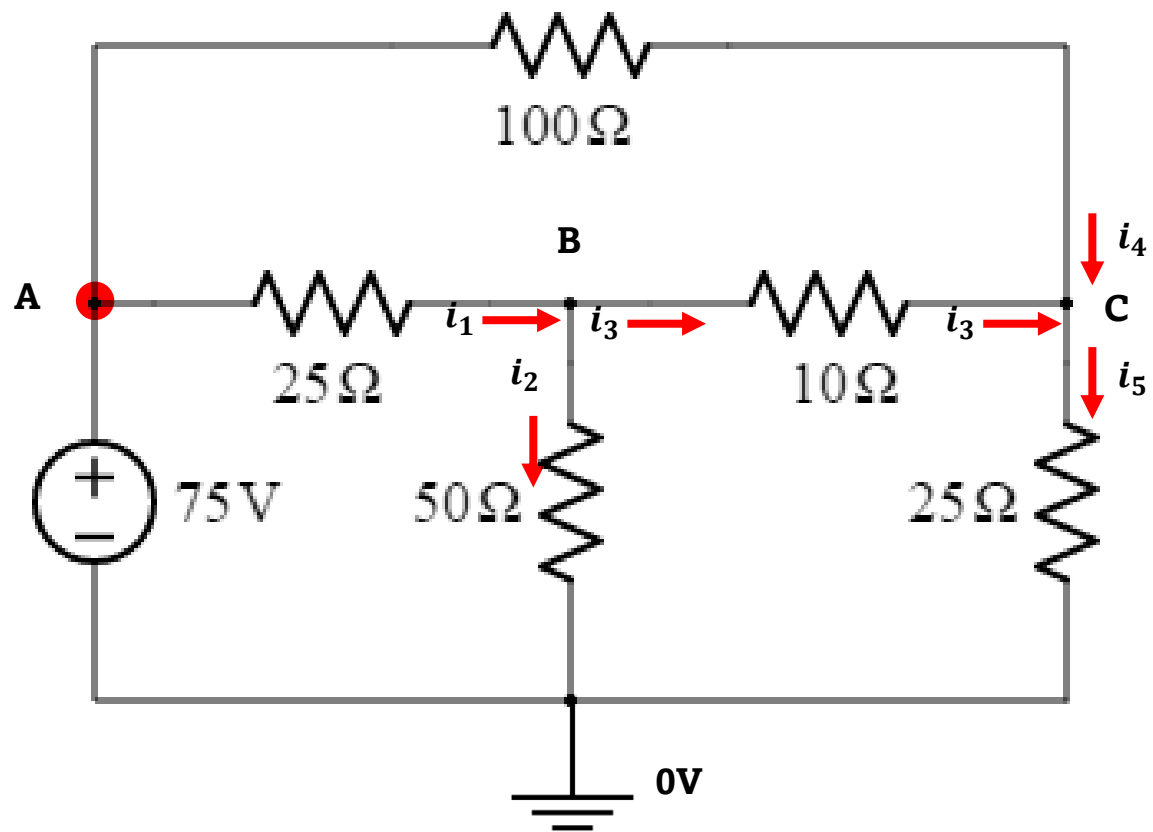STEP 4: Substitute the Ohm's law to minimize the numbers of variable.



$$A = 75V$$

$$@node B: i_1 = i_2 + i_3$$


$$\frac{A - B}{25} = \frac{B - 0}{50} + \frac{B - C}{10}$$

$$@node C: i_5 = i_3 + i_4$$

$$\frac{C - 0}{25} = \frac{B - C}{10} + \frac{A - C}{100}$$

Nodal analysis

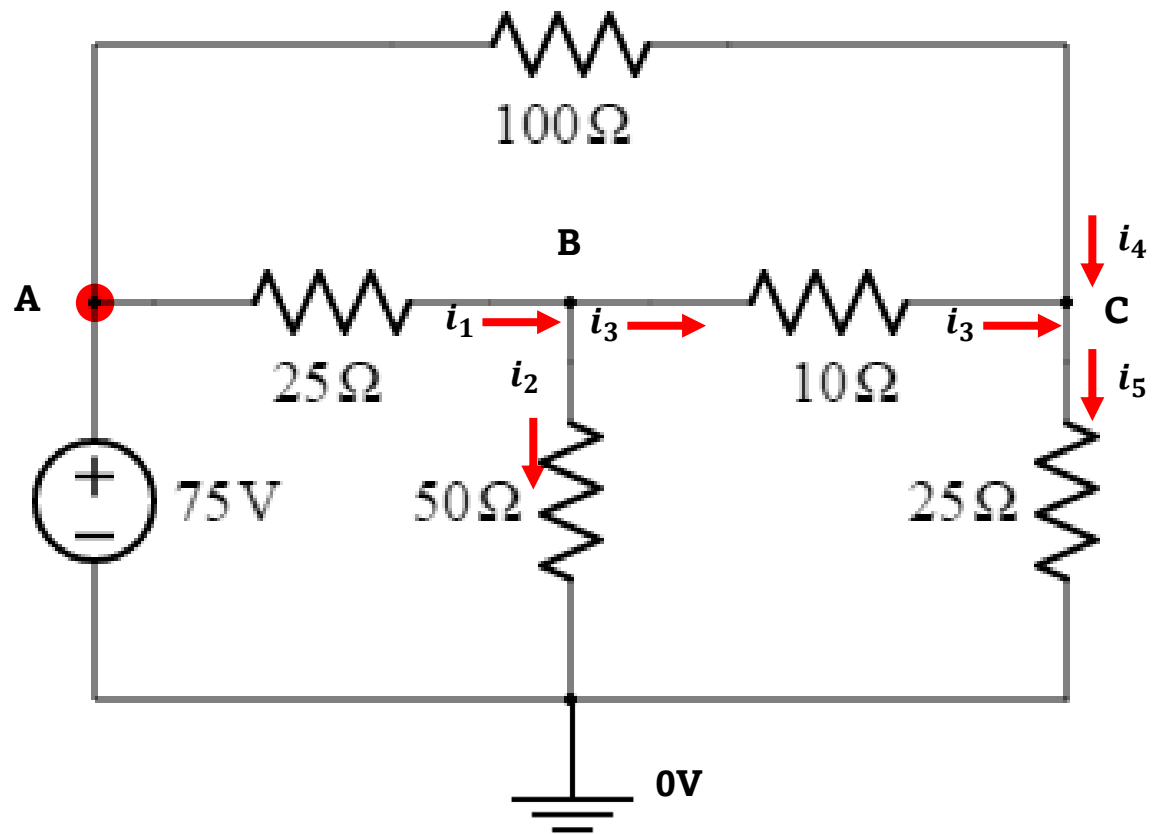STEP 5: When the number of unknown variables is equal to the number of equations means the system of equation is solvable.



$$\text{@node } B: i_1 = i_2 + i_3$$

$$\frac{75 - B}{25} = \frac{B - 0}{50} + \frac{B - C}{10}$$

$$A = 75V \mid B = 37.5V \mid C = 30V$$

$$\text{@node } C: i_5 = i_3 + i_4$$

$$\frac{C - 0}{25} = \frac{B - C}{10} + \frac{75 - C}{100}$$

