





War of Currents

Instructed By: Supun Dissanayaka




**AC &
DC**

Full Wave Rectifier

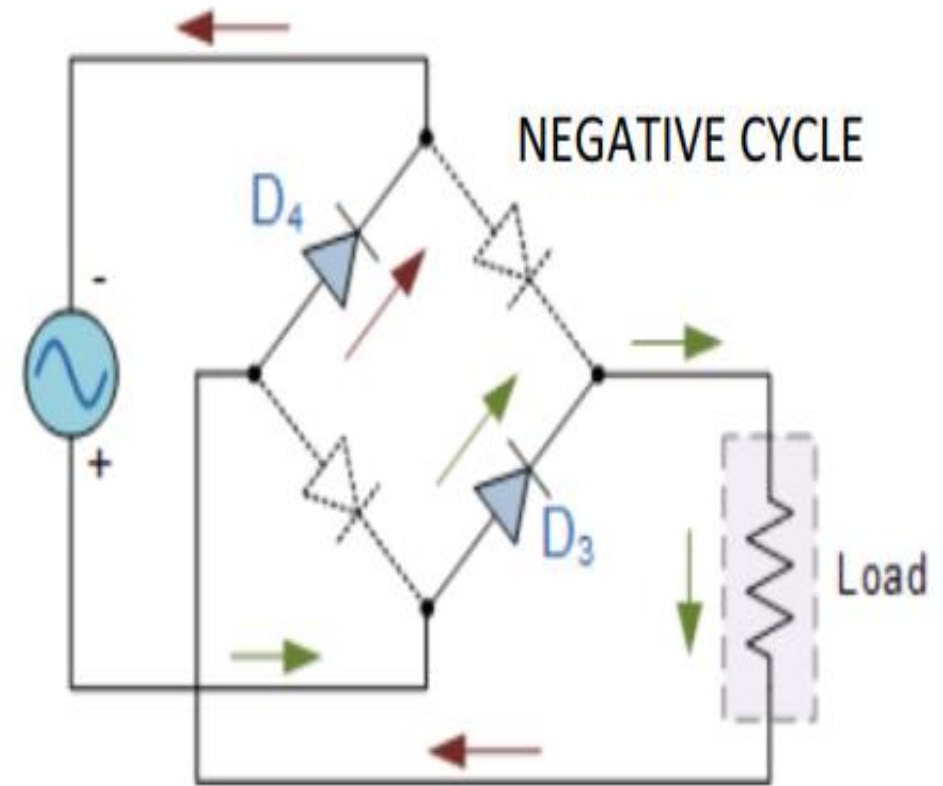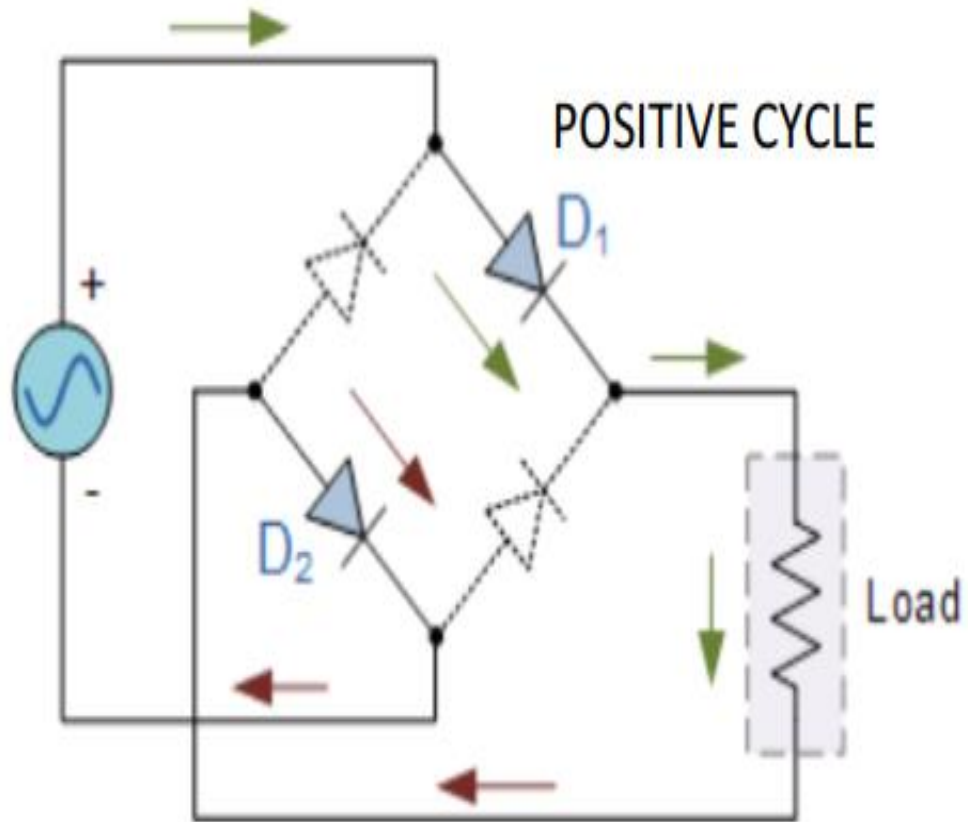

Full Wave Rectifier (Contd.)

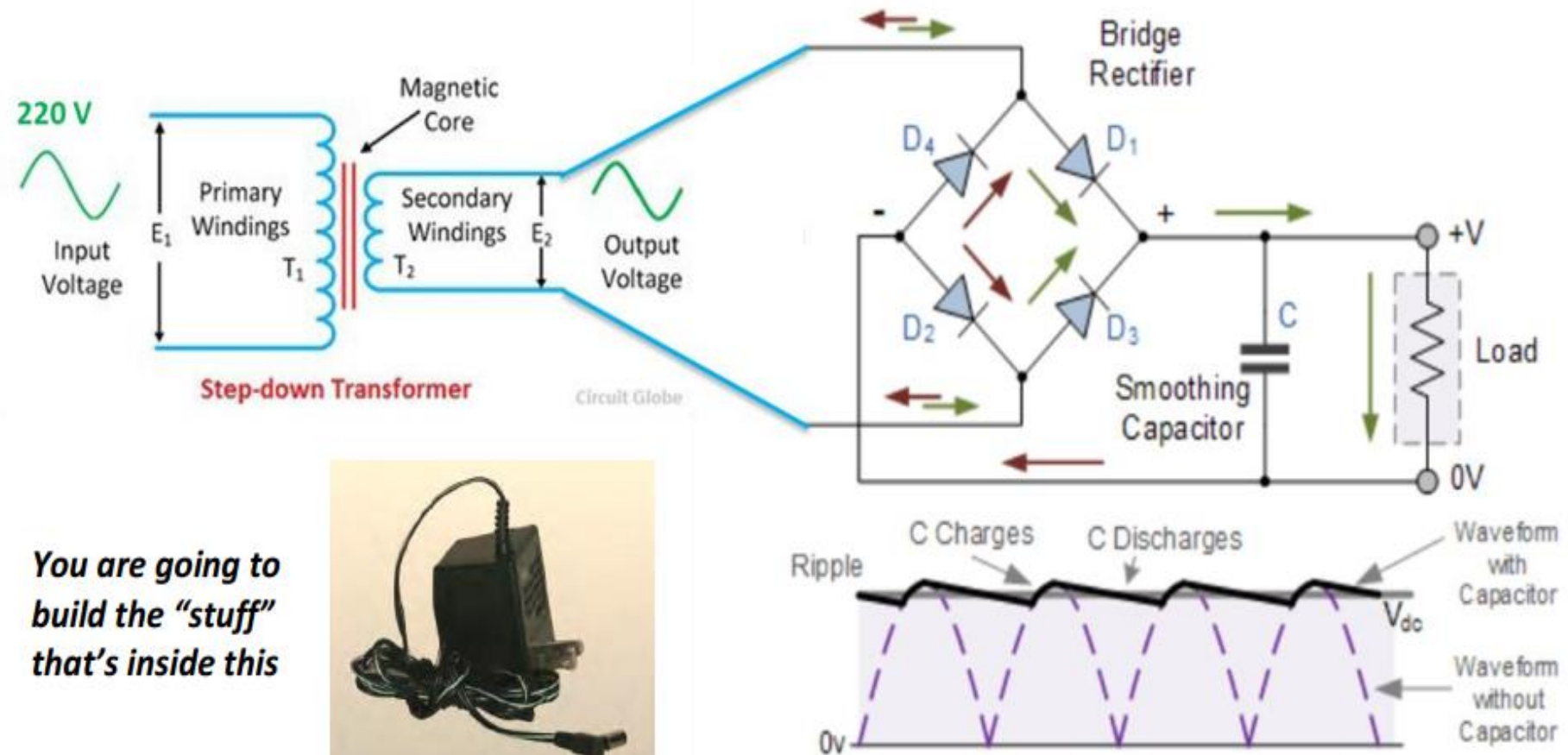

You are going to build the "stuff" that's inside this




Function Generator




Function Generator

Coaxial cable

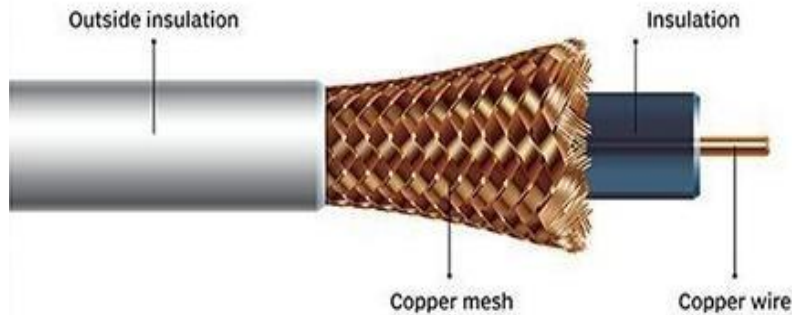

Oscilloscope

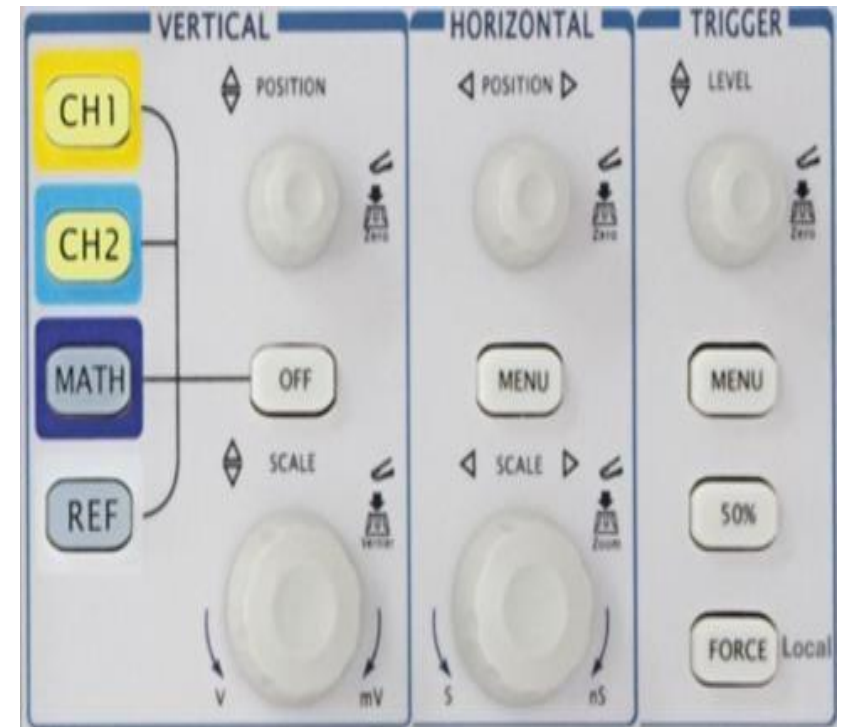

Oscilloscope (Contd.)



Thanks & have fun...